

# Characterisation of the Copenhagen Board

## End of Project Presentation

Cory Aitchison

SQA Summer Research Scholarship

Summer 2021

# Outline

## 1 Introduction

- Aims
- Equipment

## 2 Characterisation

- Operation
- Reflectometry
- Optimisation

## 3 Subprojects

- Variable Capacitors
- BB4
- Other


**Aim**

- To characterise the RF operation of the Copenhagen board
- To perform RF reflectometry on a transistor connected to the board
- To optimise the resonance circuit for resistance matching

# Copenhagen Board

The Copenhagen Board (CPH) allows for connections to a device via both DC and high-frequency circuitry, with spaces for additions of resistors, capacitors, and inductors.

- Manufactured by QDEV
- Specially designed for quantum devices
- 50 DC lines
- 16 AC lines (up to 18GHz)
- 4 multiplexed LC tank circuits

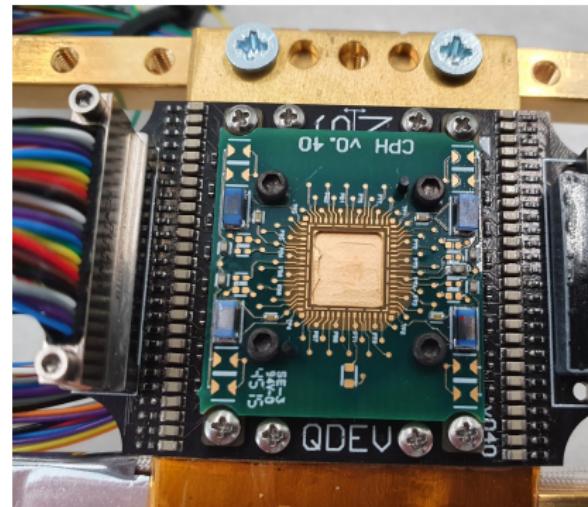

**Figure 1:** Copenhagen motherboard (black) and daughter board (green).

# Copenhagen Board

- Although CPH has been used for DC measurements, its usage under RF AC measurements is unfamiliar
- RF measurements can be beneficial because they allow for larger bandwidth (faster timescales) and lower  $1/f$  noise
- Characterisation of the board involves understanding its circuitry, resonance, and the role of the inductors, capacitors, and resistors

# MOSFET Transistor

- To characterise the CPH board, a transistor can be used as a placeholder for more complex quantum devices
- The transistor is a MOSFET
  - a *metal oxide semiconductor field-effect transistor*

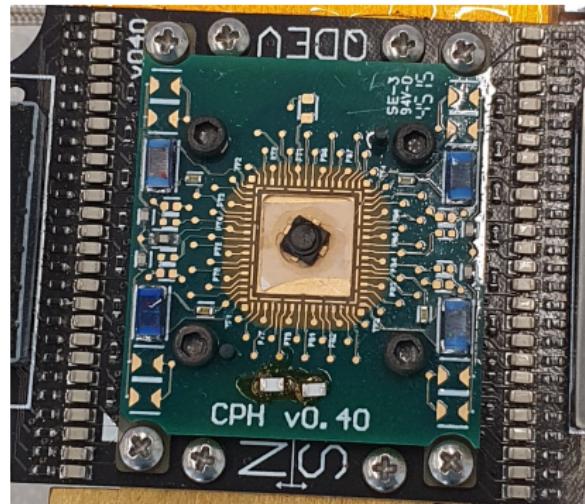


Figure 2: Transistor (black square in the gold) bonded to the daughter board.

# Transistor Characterisation

- First need to determine if the transistor is operating correctly
- 4-wire sensing was used to isolate the resistance of the transistor
- The CPH board included  $\sim 7.4\text{k}\Omega$  resistors in series

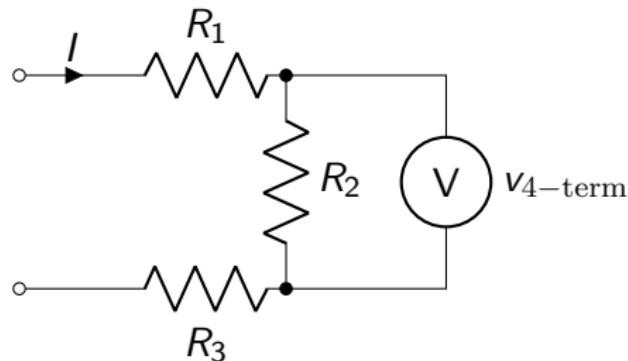


Figure 3: 4-wire resistance sensing to determine  $R_2 = V_{4-\text{term}}/I$ .

# Results - 4-wire Sensing



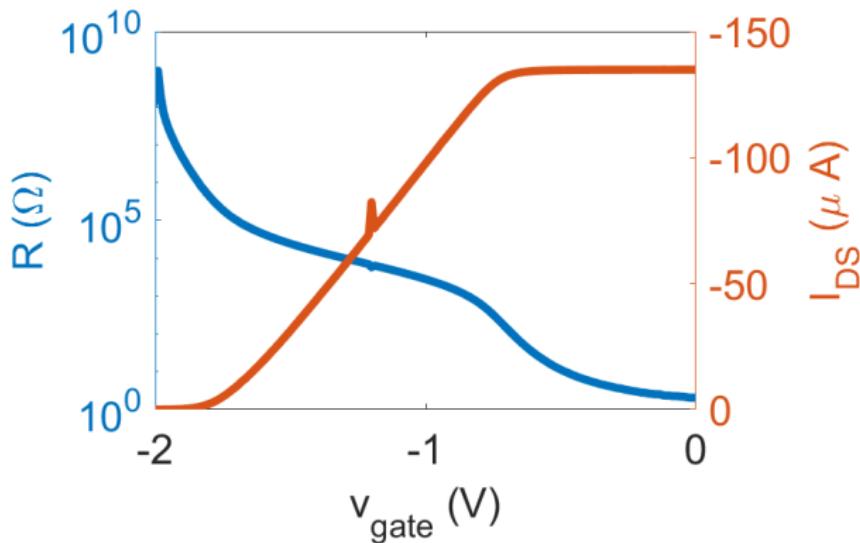


Figure 4: Current and resistance of the transistor as a function of gate voltage. Drain-source voltage is held constant at  $v_{DS} = -1 V$ .

# Results - 4-wire Sensing

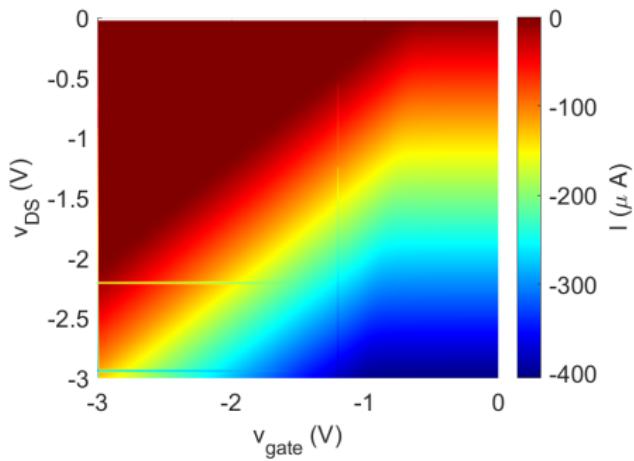

**Figure 5:** Current through the transistor as a map of drain-source and gate voltages.

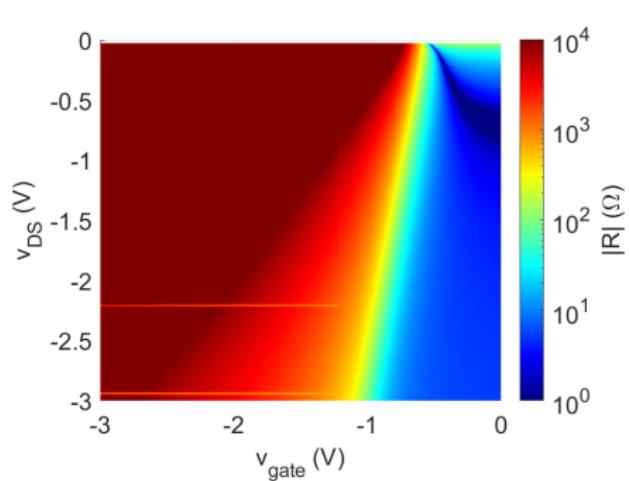

**Figure 6:** Resistance of the transistor, using 4-wire sensing

# RF Reflectometry

- Reflectometry allows us to probe the resistance of the transistor
- RF signals are inputted and reflected power is given by the following:

$$Z_t = i\omega L + \frac{1}{\frac{1}{R} + i\omega C_p} \quad (1)$$

$$\Gamma = \frac{Z_t - Z_0}{Z_t + Z_0} \quad (2)$$

$$S11 = |\Gamma|^2 \quad (3)$$

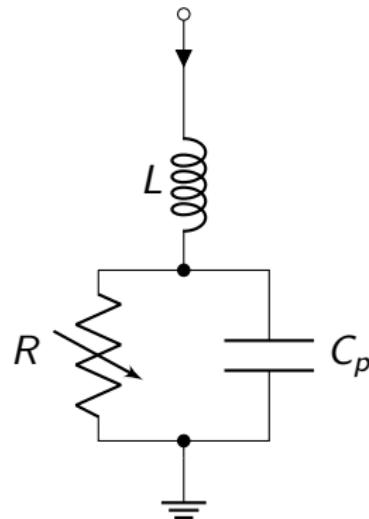


Figure 7: RLC circuit for RF reflectometry.

# RF Reflectometry

An initial RF-sweep without bonds to the transistor shows resonant peaks at frequencies corresponding to the four inductors:

Inductor	$f_{\text{res}}$ (MHz)	$L$ (nH)	$C_p$ (pF)	Status
$L1$	164	1200	0.79	-
$L2$	192	820	0.84	-
$L3$	186	560	1.3	Gate
$L4$	50	390	26	Source

**Table 1:** Measured resonant frequencies for each inductor on the Copenhagen board; Parasitic capacitance calculated using  $f_{\text{res}} = 1/2\pi\sqrt{LC_p}$ .

# RF Reflectometry Simulations

Using  $L = 390\text{nH}$ ,  $C_p = 26\text{pF}$ , we simulate theoretical reflectance using Equation 3:

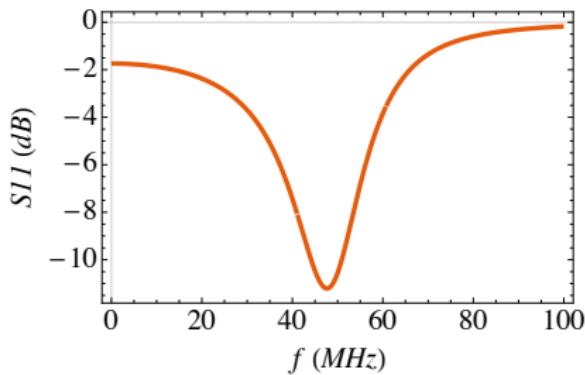


Figure 8: Simulated resonance peak at  $R = 1\text{k}\Omega$  and  $C_p = 26\text{pF}$ . Resonance occurs at  $f \approx 48\text{MHz}$ .

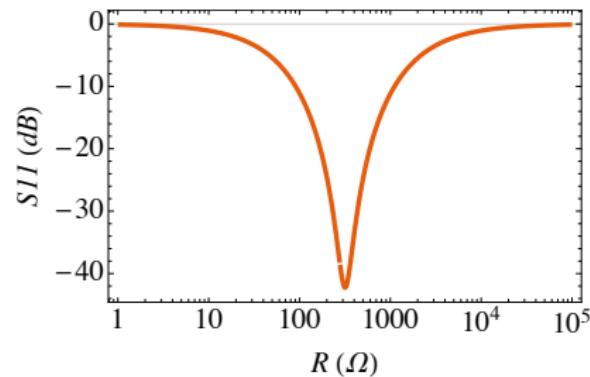


Figure 9: Simulated transfer function at resonant frequency.

# RF Reflectometry Measurements

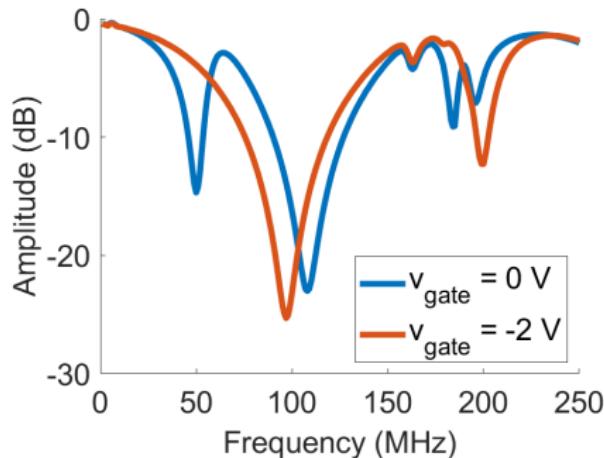


Figure 10: Resonance peaks at different gate voltages.


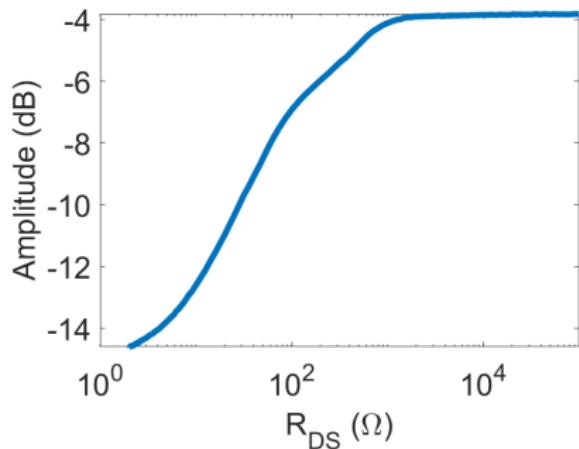


Figure 11: Transfer function at  $f = 50 \text{ MHz}$  and  $v_{DS} = -1 \text{ V}$ .


# Improved simulation model

The simple RLC circuit is not a precise representation of the actual CPH circuit; instead, the RF signal follows a path more akin to:

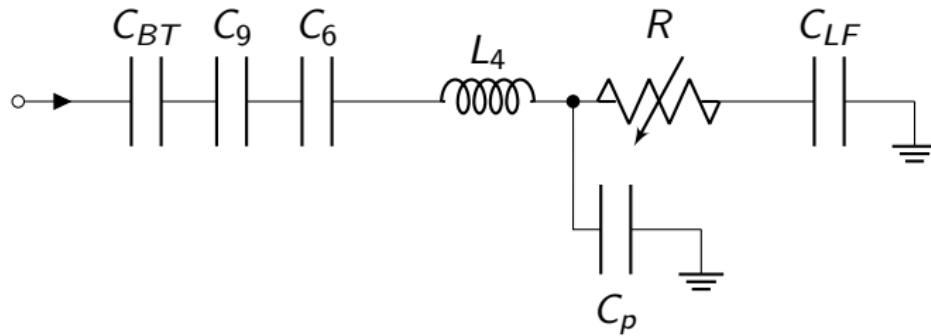

**Figure 12:** More accurate circuit diagram for the resonance circuit, with the transistor modelled as a variable resistor.

# Improved simulation model

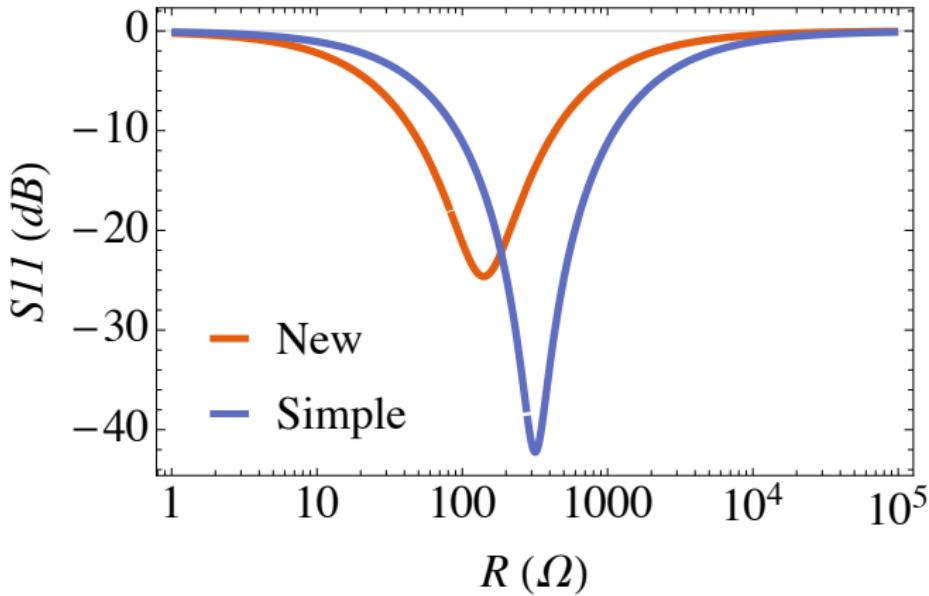

**Figure 13:** Transfer function comparison between the model from Figure 12 and that in Figure 9.

# Optimisation using Shunt Capacitors

- One issue could be that the matching resistance is too low
- By adding a shunt capacitor in parallel, we should be able to shift the matching resistance

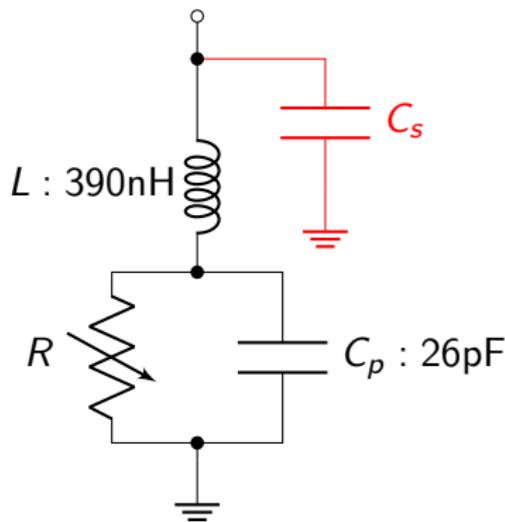


Figure 14: Circuit diagram for optimised RF reflectometry circuit.

# Simulations with Shunt Capacitors

The impedance of the new circuit (Figure 14) should be:

$$Z_t = \left[ \left( i\omega L + \frac{1}{\frac{1}{R} + i\omega C_p} \right)^{-1} + i\omega C_s \right]^{-1} \quad (4)$$

This can then be applied to Equation 3 to simulate the effects of a shunt capacitor.

# Simulations with Shunt Capacitors

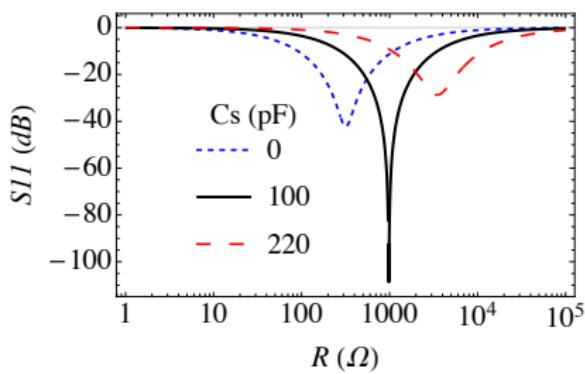


Figure 15: Comparison of transfer functions with shunt capacitors.

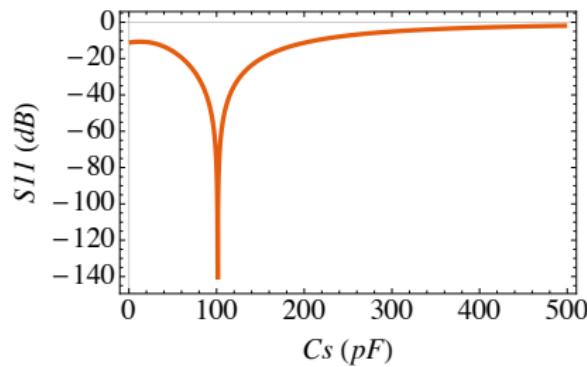


Figure 16: Simulation of  $S_{11}$  values as a function of the included shunt capacitance, at a fixed value of  $R = 1\text{k}\Omega$ .

# RF Reflectometry With A Shunt Capacitor

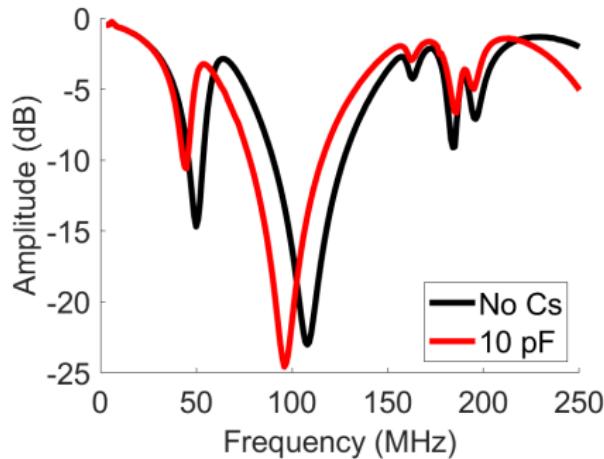


Figure 17: Resonance peaks with  $C_s = 10\text{pF}$  and  $C_s = 0$ , holding  $v_{DS} = -1\text{V}$ ,  $v_{gate} = 0$ .

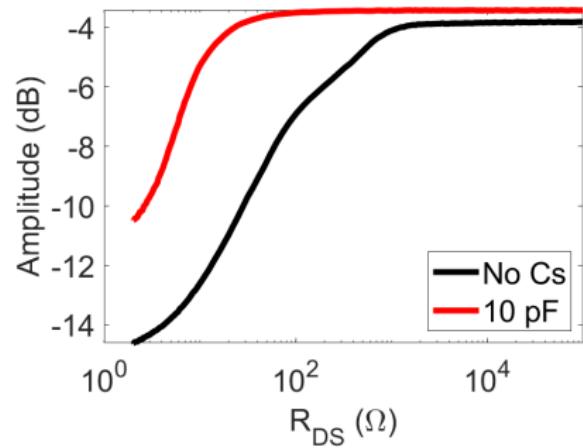


Figure 18: Transfer function at  $f = 44\text{MHz}$  with  $C_s = 10\text{pF}$  and at  $f = 50\text{MHz}$  with  $C_s = 0$ .

# RF Reflectometry With a Shunt Capacitor

- When a  $C_s = 220\text{pF}$  and a  $C_s = 1\text{nF}$  capacitor were used, no resonance peaks were observed

This may be due to:

- At larger values of  $C_s$ , the impedance of the capacitor is lower than the RLC circuit
- This creates an RF path to ground, bypassing any resonance that may occur

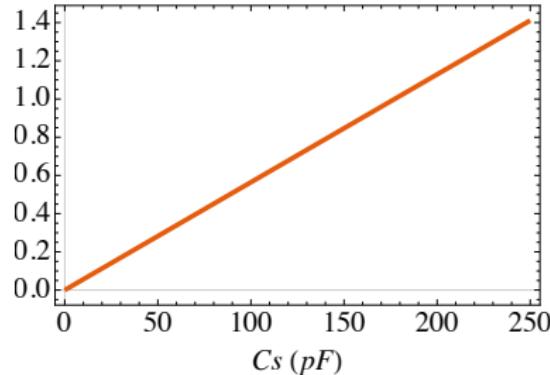


Figure 19: Ratio of RLC impedance to  $C_s$  impedance as a function of  $C_s$ , at  $f = 50\text{MHz}$ .

# Variable Capacitors

- Attempted to incorporate a variable shunt capacitor onto the CPH daughter board with the transistor
- Also attempted with a new silicon MOSFET device with smaller  $C_p$  and larger  $R$
- However was unable to measure the effective capacitance and resonance due to equipment difficulties

# Future Directions

- Beneficial to compare impedances on a device known to respond to shunt capacitances
- Repeat methods with a 100nF capacitor (the theoretical optimum)

# 4K Testing of Germanium Quantum Dot

Gate tested BB4  
(germanium  
quantum dot) at 4K  
to check that all the  
gates and ohmics  
work correctly.

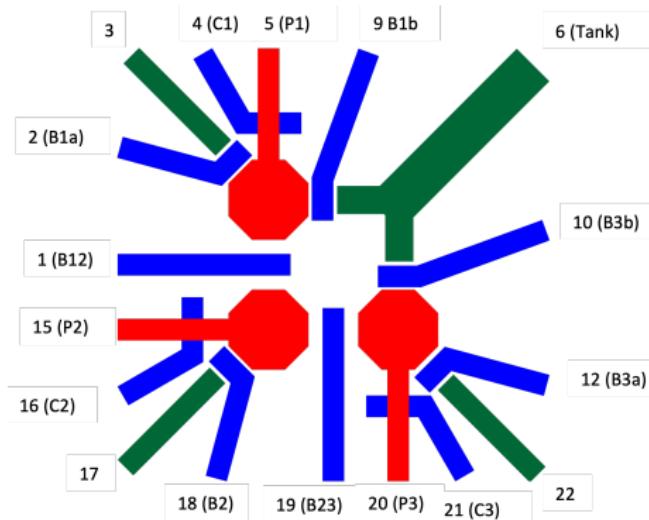


Figure 20: Schematic diagram of the gates on the device; green - ohmics; blue - barrier electrodes; red - plunger electrodes

# Other Subprojects

- Tested all contacts on two CPH boards
- Updated AWG Pulse Studio for MATLAB v2 and implemented a parametric function option
- Updated VNA driver for MATLAB v2
- Created a driver for the Keithley SM2401 source meter in MATLAB v2
- Created a driver for the Yokogawa IM7651 Variable DC Source in MATLAB v2

Thank you!

# Appendix

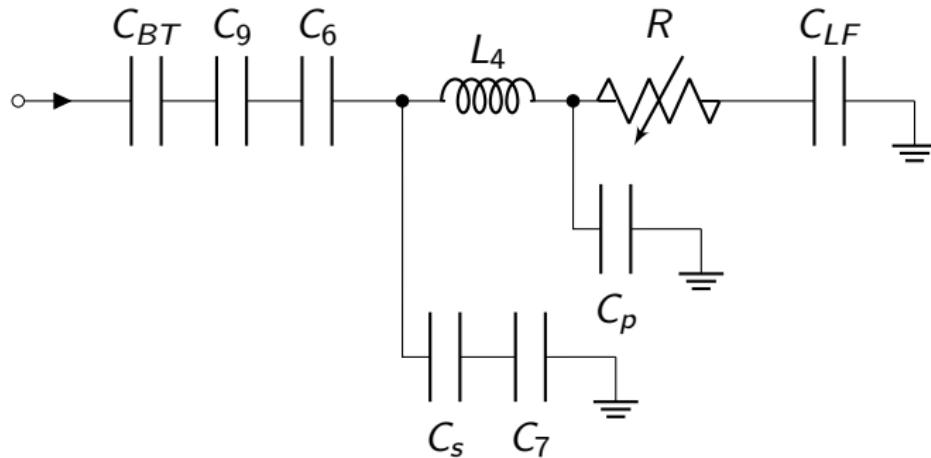


Figure 21: Figure 12 with added shunt capacitor.

# Appendix


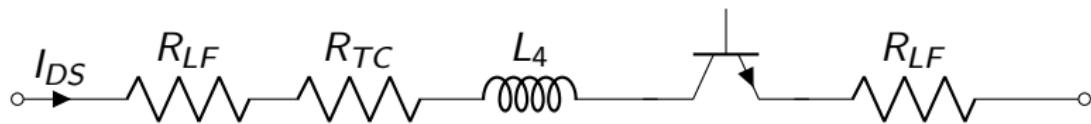




Figure 22: DC circuit supplying the transistor.

# Appendix

Copenhagen daughter board "CPH v0.40":

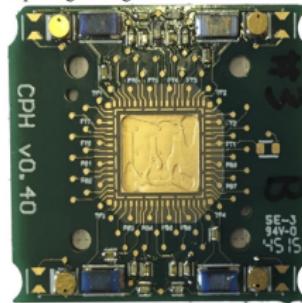

Definition of labels:

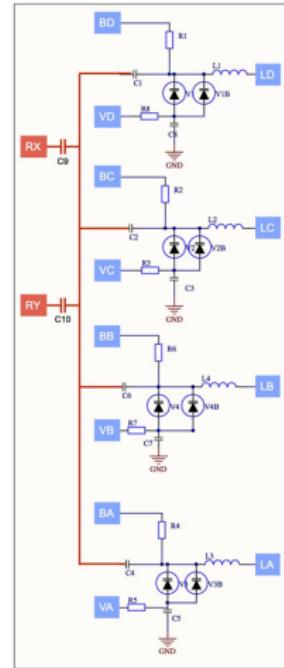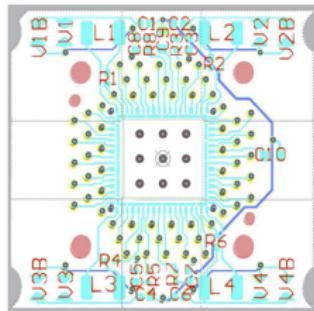

# Resonance Maps

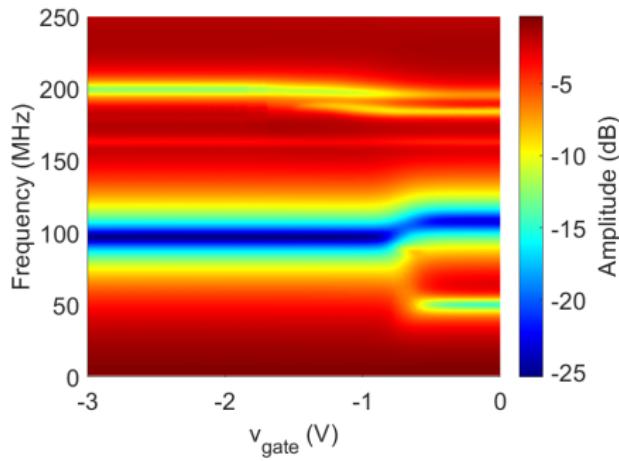


Figure 23: Resonance peaks at various  $v_{gate}$ , without a shunt capacitor.

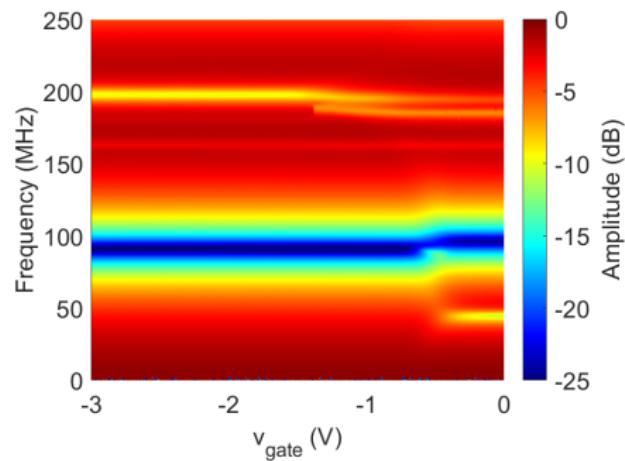


Figure 24: Resonance peaks at various  $v_{gate}$ , with  $C_s = 10\text{pF}$ .

# Transfer Functions

Transfer functions,  $f = 50$  MHz,  $C_s = 0$ ,  $V_{DS} = -1$  V  
210212rf\_005\_2021.02.15.12.44.03

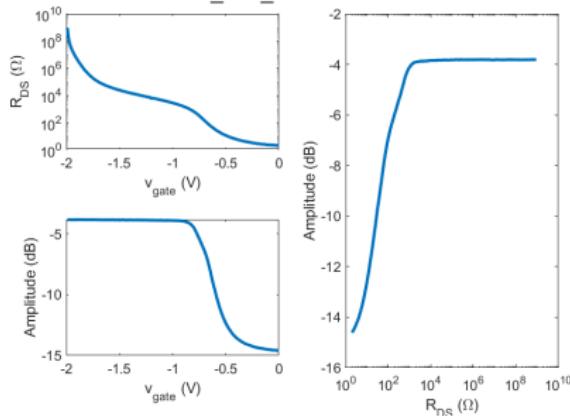


Figure 25: Transfer function at  $f = 50$  MHz and  $v_{DS} = -1$  V, with no shunt capacitor

Transfer functions,  $f = 44$  MHz,  $C_s = 10$  pF  $V_{DS} = -1$  V  
210212rf\_003\_2021.02.12.12.49.25

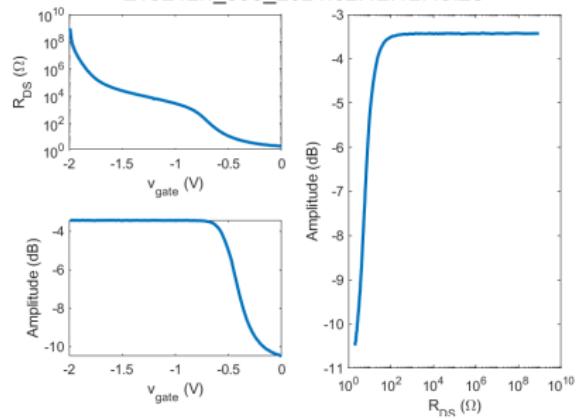


Figure 26: Transfer function at  $f = 44$  MHz, with  $C_s = 10$  pF.